

**July-22-00263**

**B. Tech. EXAMINATION, 2022**

Semester VI

LINEAR INTEGRATED CIRCUITS

EC-403

*Time : 3 Hours*

*Maximum Marks : 60*

---

*The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.*

---

**Note :** Attempt *Five* questions in all, selecting *one* question from each Sections A, B, C and D. Q. No. 9 is compulsory.

**Section A**

1. What is an OP-AMP ? Give the characteristics and equivalent circuit of a ideal OP-AMP. 10
  
2. Draw and explain the inverting and non-inverting amplifier. 10

### Section B

3. What is the limitation of an ordinary op-amp differentiator ? Draw and explain the circuit of a practical differentiator that will eliminate these limitations. **10**
4. Design a wide band reject filter having  $f_h = 400$  Hz and  $f_l = 2$  kHz having pass band gain as 2. **10**

### Section C

5. Draw the characteristics of an ideal comparator. List the different type of comparators. Explain how a non-symmetrical square wave can be obtained. **10**
6. Write a short note on Voltage to current converter. **10**

### Section D

7. Draw the circuit of a PLL AM detector and explain its operation. **10**
8. Explain FSK circuit using OP-AMP and analog multiplier. **10**

### (Compulsory Question)

9. Answer the following : **2×10=20**
  - (a) List six characteristics of an ideal op-amp.
  - (b) What is a practical op-amp ? Draw its equivalent circuit.
  - (c) Classify the oscillators.
  - (d) What do you mean by Regenerative Comparator ?
  - (e) Define slew rate and its effect.
  - (f) Give the classification of filters.
  - (g) What is the roll off rate of a first order filter ?
  - (h) List the basic building block of PLL.
  - (i) Define CMRR.
  - (j) Give the characteristics of Chebyshev filter.