

[Total No. of Questions - 9] [Total No. of Printed Pages - 3]

Dec-22-0134

EC-301 (Analog Electronics)
(ECE, EEE)

B.Tech-3rd (CBCS)

Time : 3 Hours

Max. Marks : 60

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note: Candidates are required to attempt five questions in all selecting one question from each of the section A, B, C and D of the question paper and all the subparts of the questions in section E. Use of non-programmable calculators is allowed.

SECTION A

1. (a) Calculate the break region over which the dynamic resistance of a diode is multiplied by a factor of 1000. (05)
(b) Explain how to obtain the dynamic characteristic from the static volt-ampere curve of a diode. (05)
2. (a) Derive the relation between h_{FE} and h_{fe} . (05)
(b) Discuss the two possible sources of breakdown in a transistor as the collector to emitter voltage is increased. (05)

SECTION-B

3. (a) A transformer coupling is used in the final stage of multi-stage amplifier. If the output impedance of transistor is $1k\Omega$ and the speaker has a resistance of 10Ω , find the turn ratio of the transformer so that maximum power is transferred to the load. (05)

2

EC-301

- (b) Explain Darlington pair amplifiers. (05)
4. Explain in detail high frequency model for CE amplifiers. (10)

SECTION-C

5. (a) Distinguish between class A and class B operation. (05)
(b) Derive the theoretical maximum conversion efficiency of class B power amplifier. (05)
6. A parallel resonant circuit has a capacitor of $100pF$ in one branch and inductance of $100\mu H$ plus a resistance of 10Ω in the parallel branch. Find (a) resonant frequency (b) impedance of the circuit at resonance (c) Q-factor of the circuit. (10)

SECTION-D

7. (a) The distortion in an amplifier is found to be 3%, when the feedback ratio of negative feedback amplifier is 0.04. When the feedback is removed, the distortion becomes 15%. Find the open and closed loop gain. (05)
(b) Explain the effect of lower cut-off frequency with negative feedback? (05)
8. (a) Name some optoelectronic devices. List their strengths and weaknesses in comparison to competing products / technologies. (05)
(b) Describe some measures necessary if you want to produce a high-efficiency LED. Use hand drawings to illustrate (at least) three major points. (05)

SECTION-E

9. (a) What is a crystal diode? (02)
(b) Why is Peak Inverse Voltage important in rectifier services? (02)

[P.T.O.]

- (c) In the Common-Emitter configuration, if the transistor is in the active region, then how the collector current must behave? (02)
- (d) What is utility of d.c. load line? (02)
- (e) What is the advantage of RC coupling Scheme? (02)
- (f) Why do the internal capacitances of transistor at low frequencies treated as open circuits by completely neglecting their effects in analysis? (02)
- (g) What is meant by cross over distortion in class B power amplifier and how it is corrected? (02)
- (h) What is the other name for tuned amplifier? (02)
- (i) List the four basic feedback topologies. (02)
- (j) Why silicon is not used for generation of light? (02)