

[Total No. of Questions - 9] [Total No. of Printed Pages - 2]  
Dec-22-0162

EC-404 (Pulse Shaping & Wave Generation)  
B.Tech-4th (CBCS)

Time : 3 Hours

Max. Marks : 60

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

**Note:** Attempt Five questions in all, selecting one question from each Section A, B, C and D. Section E is compulsory.

#### SECTION-A

1. What is meant by linear waveshaping? What is the unique property enjoyed by a sinusoidal input waveform? (10)
2. Obtain the expression for the output voltage of an RC high-pass filter for ramp input. Sketch the output response for  $RC/t_p \gg 1$  and  $RC/t_p \ll 1$ . (10)

#### SECTION-B

3. Sketch and describe the working of the following clipping circuits:
  - (a) Series-diode positive limiting circuit (5)
  - (b) Parallel-diode negative limiting circuit (5)
4. What is the effect of diode characteristics on clamping voltage? Explain comparators. (10)

#### SECTION C

5. Sketch the circuit of a simple diode unidirectional sampling gate and describe its functioning with neat waveforms. Explain the effect of the higher voltage level  $-V_2$  of the control input on the output of the circuit. (10)
6. Explain the basic operating principle of sampling gates. (10)

2

#### SECTION D

EC-404

7. Describe the effect of loop gain on the behaviour of the Schmitt trigger circuit with neat sketches of the transfer characteristic. (10)
8. Write a short note on Digital to Analog Converter. (10)

#### SECTION E

9. Answer the following: (10×2=20)
  - a. What is the condition for RC high-pass filter to act as good differentiator?
  - b. Give some general features of a time base signal.
  - c. What is the purpose of linear waveshaping?
  - d. What are the applications of 555 timer IC?
  - e. When does a transistor Schmitt trigger circuit fail to convert a periodic waveform into a square waveform?
  - f. Which components are primary responsible for the occurrence of the quasistable state in a collector coupled monostable multivibrator?
  - g. How does flash ADC work?
  - h. A 5-bit ladder has a digital input of 11010. Assuming that 0 corresponds to 0V and 1 corresponds to +10 V. What will be its output?
  - i. List different types of clippers.
  - j. Write the application of Digital to Analog converters.